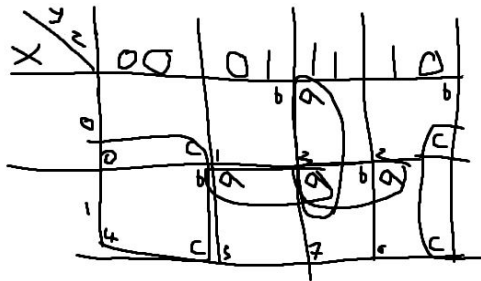


Marco Flores
Cs231
A3 May 6 2019

1)


x	y	z	a	b	c
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0




$$a = xz + xy + yz$$

$$b = xy'z' + x'yz' + xyz + x'y'z$$

$$c = z'$$

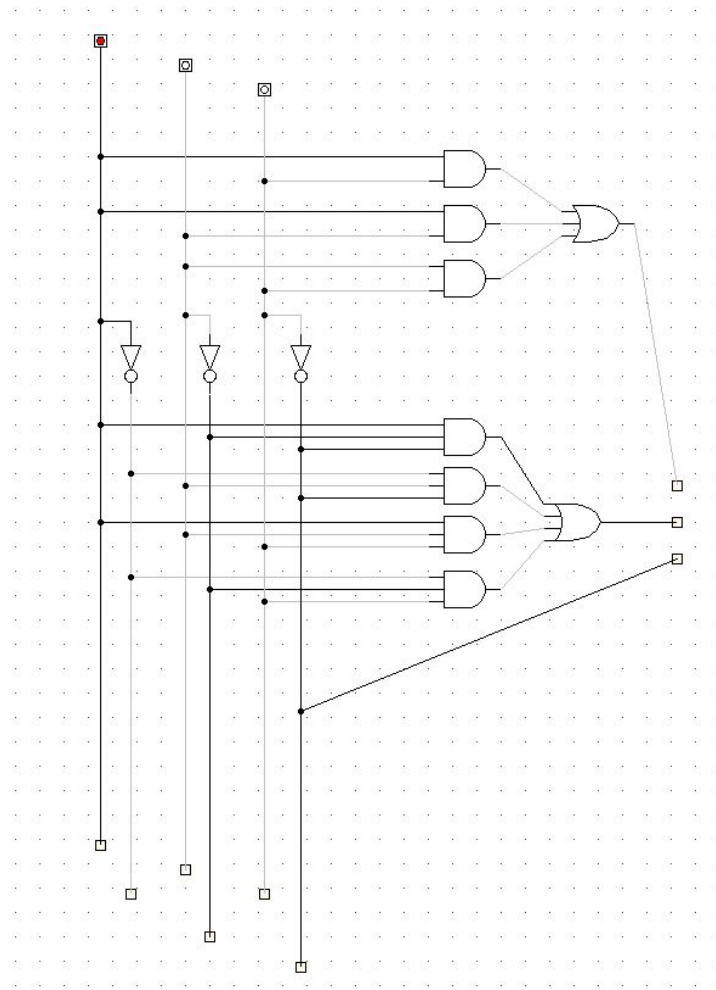

*2) flip bits then add one.

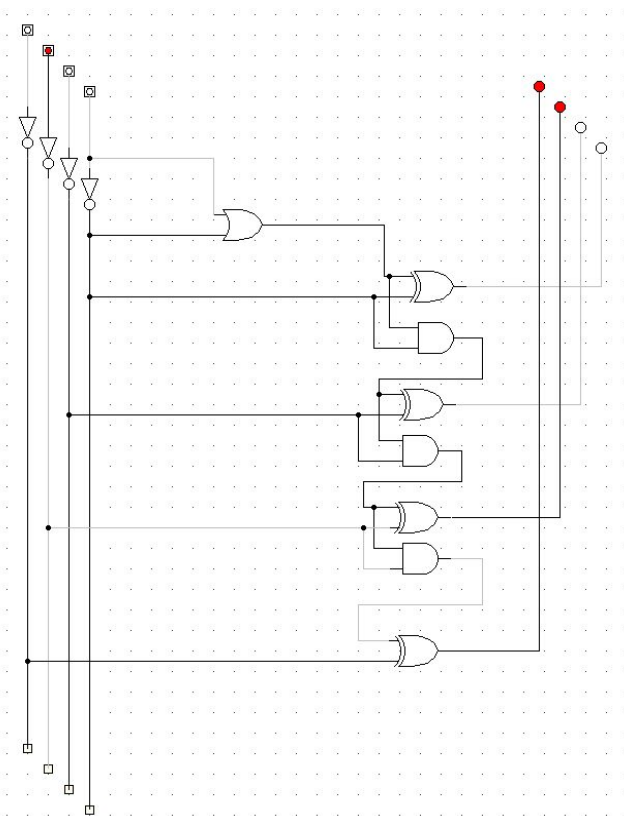


3) We can derive a truth table with the given equation $Q'(t+1) = J'Q' + KQ$ and compare if it is the same as $Q'(t+1)$ from a JK flip flop Since we know the jk truth table is

J	K	$Q(t+1)$	$Q'(t+1)$
0	0	Q	Q'
0	1	0	1
1	0	1	0
1	1	Q'	Q

J	K	Q	$Q'(t+1)$	Same as JK? Yes
0	0	0	1	J=0 K=0 Q=0 then Q' which is the same as $Q'(t+1)$, True
0	0	1	0	J=0 K=0 Q=1 then Q' which is the same as $Q'(t+1)$, True
0	1	0	1	J=0 K=1 Q=0 then 1 which is the same as $Q'(t+1)$, True
0	1	1	1	J=0 K=1 Q=1 then 1 which is the same as $Q'(t+1)$, True
1	0	0	0	J=1 K=0 Q=0 then 0 which is the same as $Q'(t+1)$, True
1	0	1	0	J=1 K=0 Q=1 then 0 which is the same as $Q'(t+1)$, True
1	1	0	0	J=1 K=1 Q=0 then Q which is the same as $Q'(t+1)$, True
1	1	1	1	J=1 K=1 Q=1 then Q which is the same as $Q'(t+1)$, True


Since $Q'(t+1)$ derived from the equation is the same as $Q'(t+1)$ from a JK flip flop for all cases of J,K, and Q then $Q'(t+1) = J'Q' + KQ$ is the characteristic equation for the complement output of a JK flip flop.

4a)

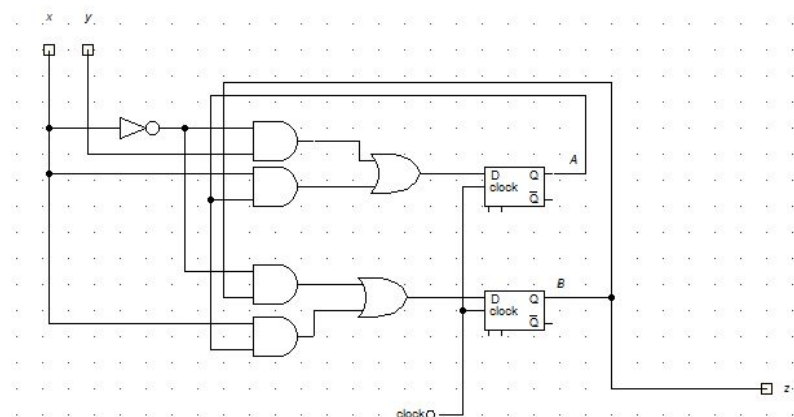

4b)

x	y	A(t)	B(t)	A(t+1)	B(t+1)	z
0	0	0	0	0	0	0
0	0	0	1	0	1	1
0	0	1	0	0	0	0
0	0	1	1	0	1	1
0	1	0	0	1	0	0
0	1	0	1	1	1	1
0	1	1	0	1	0	0
0	1	1	1	1	1	1
1	0	0	0	0	0	0
1	0	0	1	0	0	1
1	0	1	0	1	1	0
1	0	1	1	1	1	1
1	1	0	0	0	0	0
1	1	0	1	0	0	1
1	1	1	0	1	1	0
1	1	1	1	1	1	1

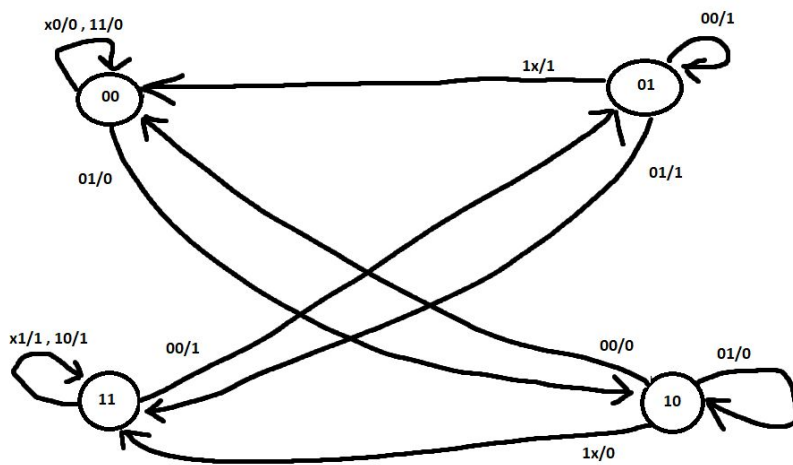


4c)

5)

State table:


A(t)	B(t)	A(t+1)	B(t+1)	Ta	Tb
0	0	0	1	0	1
0	1	1	0	1	1
1	0	0	0	1	0
1	1	0	0	1	1

State Diagram:

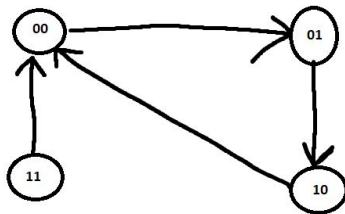

6a)

x	A(t)	B(t)	A(t+1)	B(t+1)	Ja	Ka	Jb	Kb
0	0	0	0	0	0	1	0	0
0	0	1	0	1	0	0	0	0
0	1	0	0	0	0	1	0	1
0	1	1	1	0	0	0	0	1
1	0	0	1	1	1	1	1	0
1	0	1	1	1	1	0	1	0
1	1	0	0	1	1	1	1	1
1	1	1	1	0	1	0	1	1

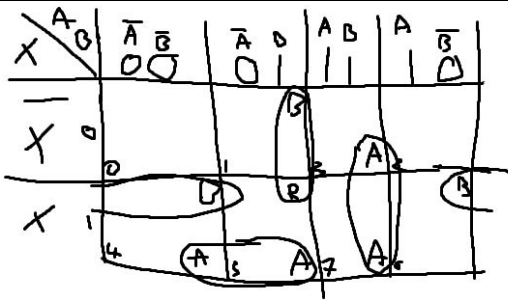

$$A(t+1) = xA' + AB$$

$$B(t+1) = xB' + A'B$$

6b)

